

Indian Institute of Technology (IIT-Kharagpur)

AUTUMN Semester, 2024

COMPUTER SCIENCE AND ENGINEERING

Computer Organization Laboratory

Verilog Assignment 2

INSTRUCTIONS: Please see the question and develop the design in a step by step fashion. Special credit would be given for designs which are modular.

Design of a 4-bit Parallel-load Linear Feedback Shift Register (LFSR)

About the Design:

The objective is to design a synchronous sequential circuit using four D flip-flops, which when loaded by a non-zero initial vector (called **seed**), cycles through all the 15 non-zero binary vectors before returning to the initial vector (the **seed**). Thus this can be used as a modulo-15 counter. The only combinational blocks required are XOR gates. This forms a very useful structure, commonly known as *Linear Feedback Shift Register* (LFSR), and has extensive use in digital circuits, communication theory, etc.

Details of the Circuit:

The design is a synchronous sequential circuit using four D flip-flops connected as shown in **Figure 1**. The flip-flops can be initialized with a **seed** by using four multiplexers as shown. When the select line of the multiplexer **sel** is made 0, the bits of the **seed** vector are passed to the D inputs of the flip-flops. For each of the three flip-flops on the right, when **sel** = 1, the output of the DFF to its left is applied to the input. For the left-most DFF, the bit to be shifted in when the **sel** = 1, is computed by XORing the outputs of the two DFFs on the right as shown.

The wire names are mentioned in the diagram to help in your design. Also note that DFFs will have an asynchronous reset input **rst**. For the purpose of demonstration on the FPGA board, you need to use a very slow clock (frequency ~ 1 Hz); therefore, the input clock is to be divided as required.

The Assignment:

For the design of the LFSR and demonstrate its working, proceed with the following steps.

1. Design the circuit using Verilog in a modular fashion. Your design should have a **top-level** module which instantiates separate sub-modules for:
 - (a) D flip-flops (DFF)
 - (b) Multiplexers (MUX)
 - (c) Clock-Divider (CLKDiv)

The inputs of the design are: (i) 4-bit **seed**, (ii) **rst**, (iii) **sel**, and (iv) **clk** (generated internally in the board and later divided by your CLKDiv module). The output will be a 4-bit state of the flip-flops, denoted by **state[3:0] = {w2,w3,w4,w5}**.

2. Write a UCF file for the design, ensuring that the 4-bit **seed**, **rst**, and **sel** inputs are provided from the switches on your board. The output state must be visualised in the LEDs of your board.
3. Download the design's bit file onto the FPGA board and demonstrate the evolution of the LFSR using the slow clock. Load the LFSR by the non-zero seed 1111, and verify that it comes back to the same state after 15 clock ticks. The state transitions of the LFSR will be as follows: 1111 → 0111 → 0011 → 0001 → 1000 → 0100 → 0010 → 1001 → 1100 → 0110 → 1011 → 0101 → 1010 → 1101 → 1110 → 1111.

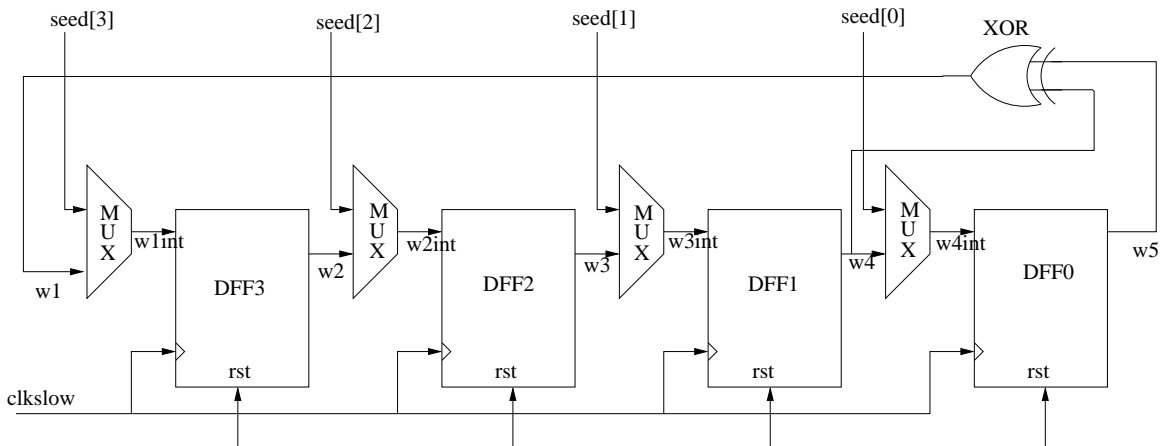


Figure 1: Schematic diagram of the 4-bit LFSR